

Worksheet: Electricity: Circuits and their Components

Haryana State Board · Class 7 · Science · 4 questions · 10 marks

Name: _____	Date: _____	Score: _____ / 10
-------------	-------------	-------------------

Q1. A bulb does not glow in a circuit. Name two possible reasons. *[2 marks]*

Q2. Why is copper used in wires? *[2 marks]*

Q3. Why are plug covers made of plastic? *[3 marks]*

Q4. What is the role of a switch? *[3 marks]*
