

## Worksheet: Electricity: Circuits and their Components

Odisha State Board · Class 7 · Science · 4 questions · 10 marks

Name: \_\_\_\_\_

Date: \_\_\_\_\_

Score: \_\_\_\_\_ / 10

**Q1.** A bulb does not glow in a circuit. Name two possible reasons. *[2 marks]*

---

---

---

**Q2.** Why is copper used in wires? *[2 marks]*

---

---

---

**Q3.** Why are plug covers made of plastic? *[3 marks]*

---

---

---

**Q4.** What is the role of a switch? *[3 marks]*

---

---

---